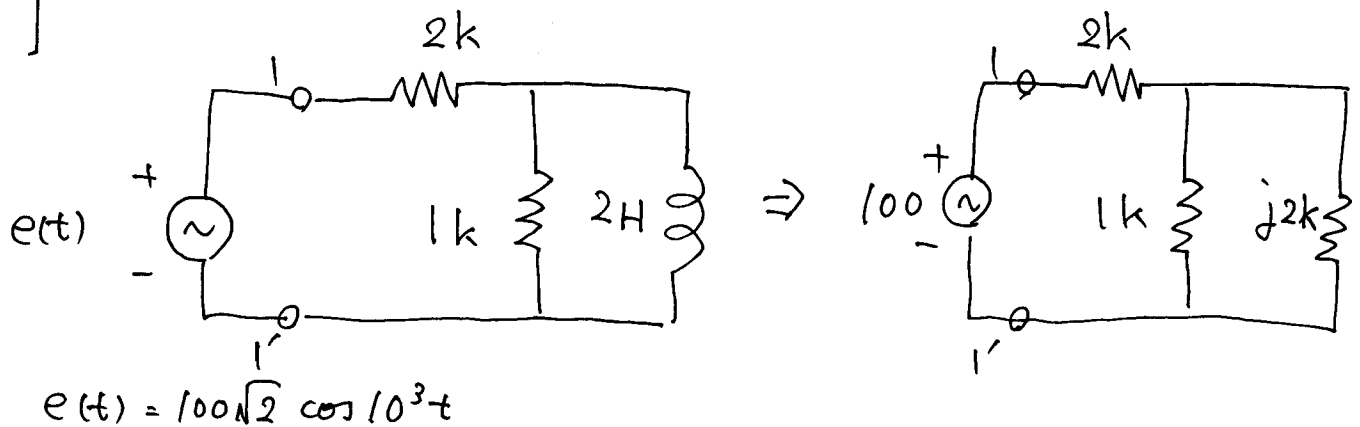


[1]



(a) 1-1' から右側をみた合成 $\bar{Z}$

$$\begin{aligned} \bar{Z} &= 2k + \frac{1k \cdot j2k}{1k + j2k} \\ &= 2k + \frac{4k}{5} + j\frac{2k}{5} \\ &= \frac{14k}{5} + j\frac{2k}{5} \quad (\text{答}) \rightarrow \frac{2}{5}(7+j) [k\Omega] \quad (\text{答}) \end{aligned}$$


(b)

$$\begin{aligned} \dot{W} &= \dot{V} \bar{I} = \frac{|\dot{V}|^2}{\bar{Z}} = 100^2 \cdot \frac{1}{\frac{2}{5}(7-j) \times 10^3} \\ &= \frac{7}{2} + j\frac{1}{2} \end{aligned}$$


$$\therefore P = \frac{7}{2} [W], \quad Q = \frac{1}{2} [\text{var}] \quad (\text{答})$$

$$\cos \phi = \frac{\frac{7}{2}}{\sqrt{(\frac{7}{2})^2 + (\frac{1}{2})^2}} \approx 0.99 \quad (\text{答})$$


[2]

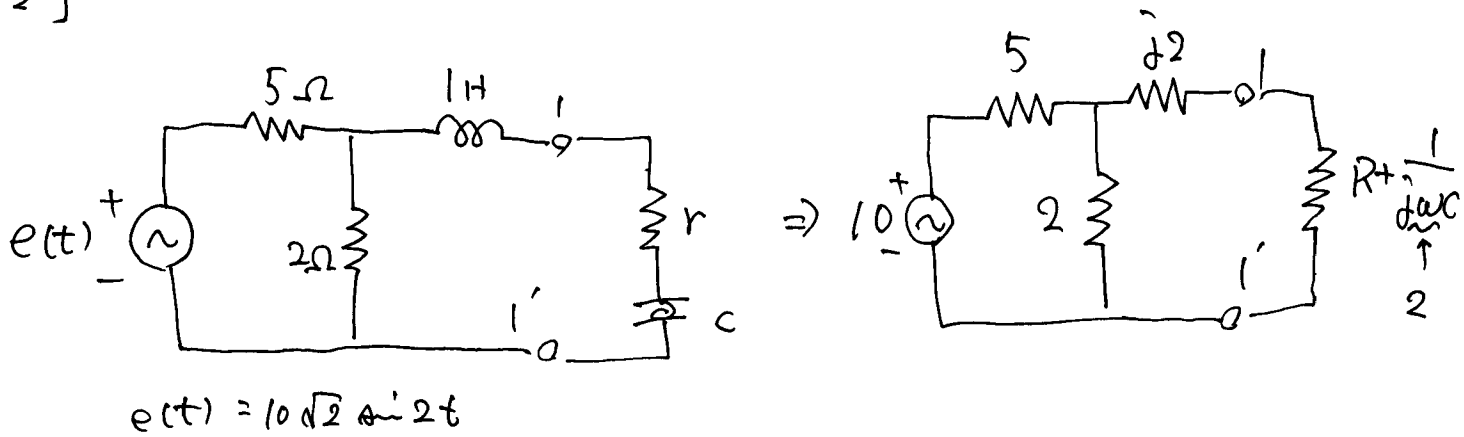

(a) $1-1'$ から左を見て、テブナンの方法で

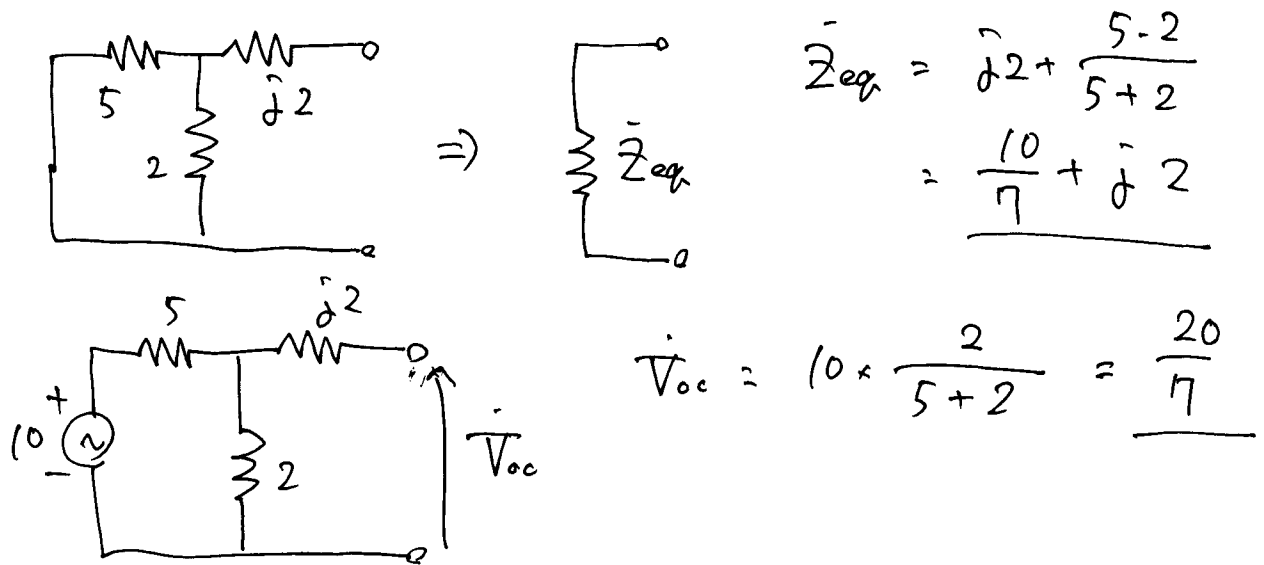


等価回路

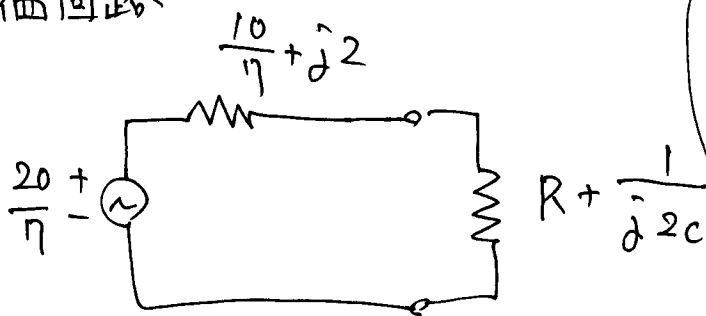

$$\therefore R = \frac{10}{7}, \quad \frac{-1}{j2C} = j2$$

$$\therefore r = \frac{10}{7} \Omega, \quad C = \frac{1}{4} F \quad (\text{答})$$

(b) 2 のとき、


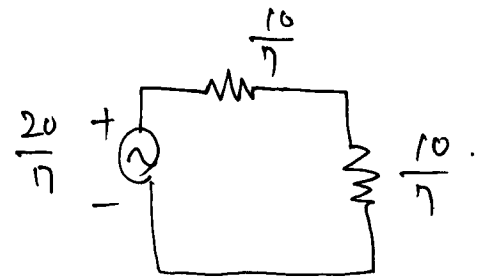


$$\therefore P_r = \frac{\left(\frac{20}{7}\right)^2}{\frac{20}{7}} \times \frac{1}{2}$$

$$= \frac{10}{7} [W]$$

(答)

[3]

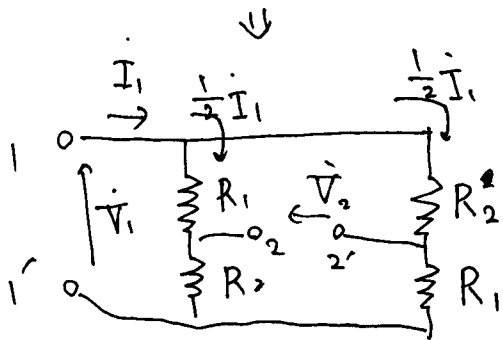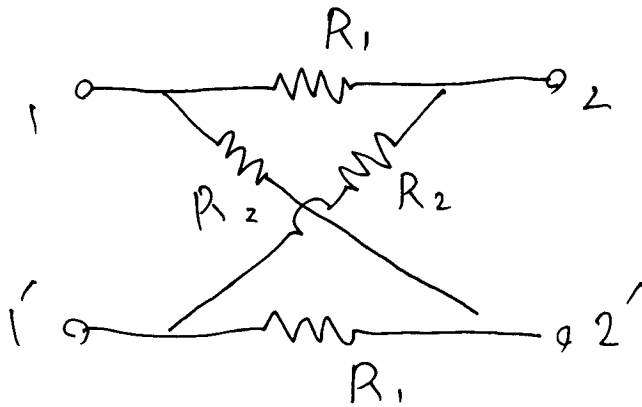

左図より. $\dot{V}_1 = \frac{R_1 + R_2}{2} \dot{I}_1$

$$\therefore \dot{Z}_{11} = \left. \frac{\dot{V}_1}{\dot{I}_1} \right|_{\dot{I}_2=0} = \frac{R_1 + R_2}{2}$$

$$\dot{V}_2 = \frac{R_2 - R_1}{2} \dot{I}_1$$

$$\therefore \dot{Z}_{21} = \left. \frac{\dot{V}_2}{\dot{I}_1} \right|_{\dot{I}_2=0} = \frac{R_2 - R_1}{2}$$


対称性より.

$$\underline{Z} = \begin{bmatrix} \frac{R_1 + R_2}{2} & \frac{R_2 - R_1}{2} \\ \frac{R_2 - R_1}{2} & \frac{R_1 + R_2}{2} \end{bmatrix} \quad (\text{答})$$

$$\underline{Y} = \underline{Z}^{-1} = \frac{1}{\left(\frac{R_1 + R_2}{2}\right)^2 - \left(\frac{R_2 - R_1}{2}\right)^2} \begin{bmatrix} \frac{R_1 + R_2}{2} & \frac{R_1 - R_2}{2} \\ \frac{R_1 - R_2}{2} & \frac{R_1 + R_2}{2} \end{bmatrix}$$

$$= \begin{bmatrix} \frac{R_1 + R_2}{2R_1R_2} & \frac{R_1 - R_2}{2R_1R_2} \\ \frac{R_1 - R_2}{2R_1R_2} & \frac{R_1 + R_2}{2R_1R_2} \end{bmatrix} \quad (\text{答})$$

[4] 2-ポート表現にしよう

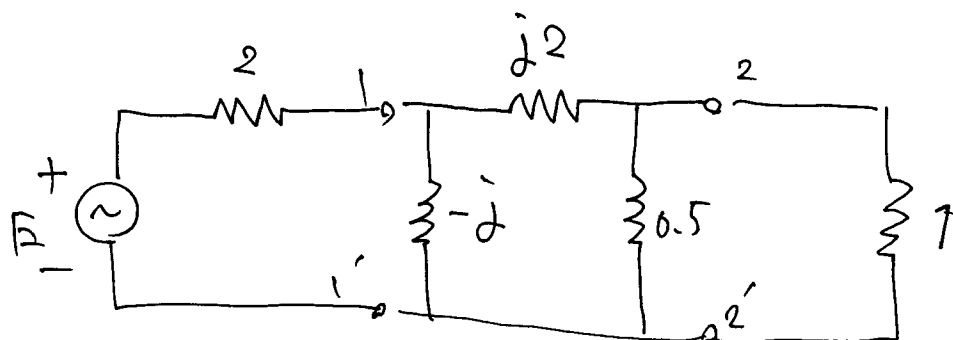


$$(a) F = \begin{bmatrix} 1 & 0 \\ j & 1 \end{bmatrix} \begin{bmatrix} 1 & j2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 2 & 1 \end{bmatrix} = \begin{bmatrix} 1+j4 & j2 \\ -2+j & -1 \end{bmatrix} \quad (\text{答})$$

$$(b) \hat{Z}_{in} = \frac{\hat{A}\hat{Z}_e + \hat{B}}{\hat{C}\hat{Z}_e + \hat{D}} = \frac{(1+j4) \cdot 1 + j2}{(-2+j) \cdot 1 - 1} = \frac{1+j6}{-3+j} \quad (\text{答})$$

$\uparrow \frac{1}{10}(3-j19)$
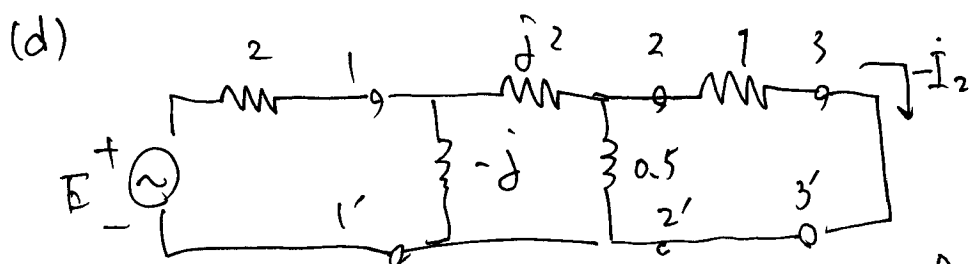
$$(c) \hat{I}_1 = \frac{E}{2 + \frac{1+j6}{-3+j}} = \frac{-3+j}{-5+j8} E = \frac{1}{89} (23+j19) E \quad (\text{答})$$



上図のポートに考えよ。(-1' - 3-3'間)。

$$D = \left. \frac{\hat{I}_1}{-\hat{I}_2} \right|_{\hat{V}_2=0} \quad (*)$$

$$F = \begin{bmatrix} 1+j4 & j2 \\ -2+j & -1 \end{bmatrix} \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix}$$

↓

$$D = -3+j$$

$$\hat{I} = -\hat{I}_2 = \frac{\hat{I}_1}{D}$$

$$= \frac{1}{-3+j} \cdot \frac{-3+j}{-5+j8} E$$

$$= \frac{1}{-5+j8} E = \frac{E}{89} (-5-j8) \quad (\text{答})$$